

# COL215 - Assignment 2

## Design overview of Digital clock


Inputs: 1) Clock ( $10\text{ MHz}$ ,  $10^7$  cycles per sec)  
2) 5-push buttons of different functions/features

Output: 4 seven-segment displays, each one displaying 4 out of 6 digits of time in 24 hr format i.e. hh:mm:ss, probably with a decimal point for denoting mode of display

Denote displays as  $d1, d2, d3, d4$  and push-buttons as  $b1, b2, b3, b4, b5$

## User interface:

① Seven-segment display:

 


single digit display

• ← optional decimal point

A, B, C, D, E, F, G → segments (in bits)  
P → decimal point (bit)



## ② Digital Clock

 

Display Mode/  
Time Select Mode

Mode Selector  
~~hh:mm~~ or  
~~mm:ss~~

In display mode of digital clock,

- b1 → button for hh:mm display format
- b2 → button for mm:ss display format
- b3 → reset button (resets the clock to 00:00:00)


In time setting / time selecting mode,

- b1 → up-counter button for digit d1
- b2 → up-counter button for digit d2
- b3 → up-counter button for digit d3
- b4 → up-counter button for digit d4

The max count of these digits depends upon the format of display i.e. whether the digit represents hour, minute or second



# State Diagram

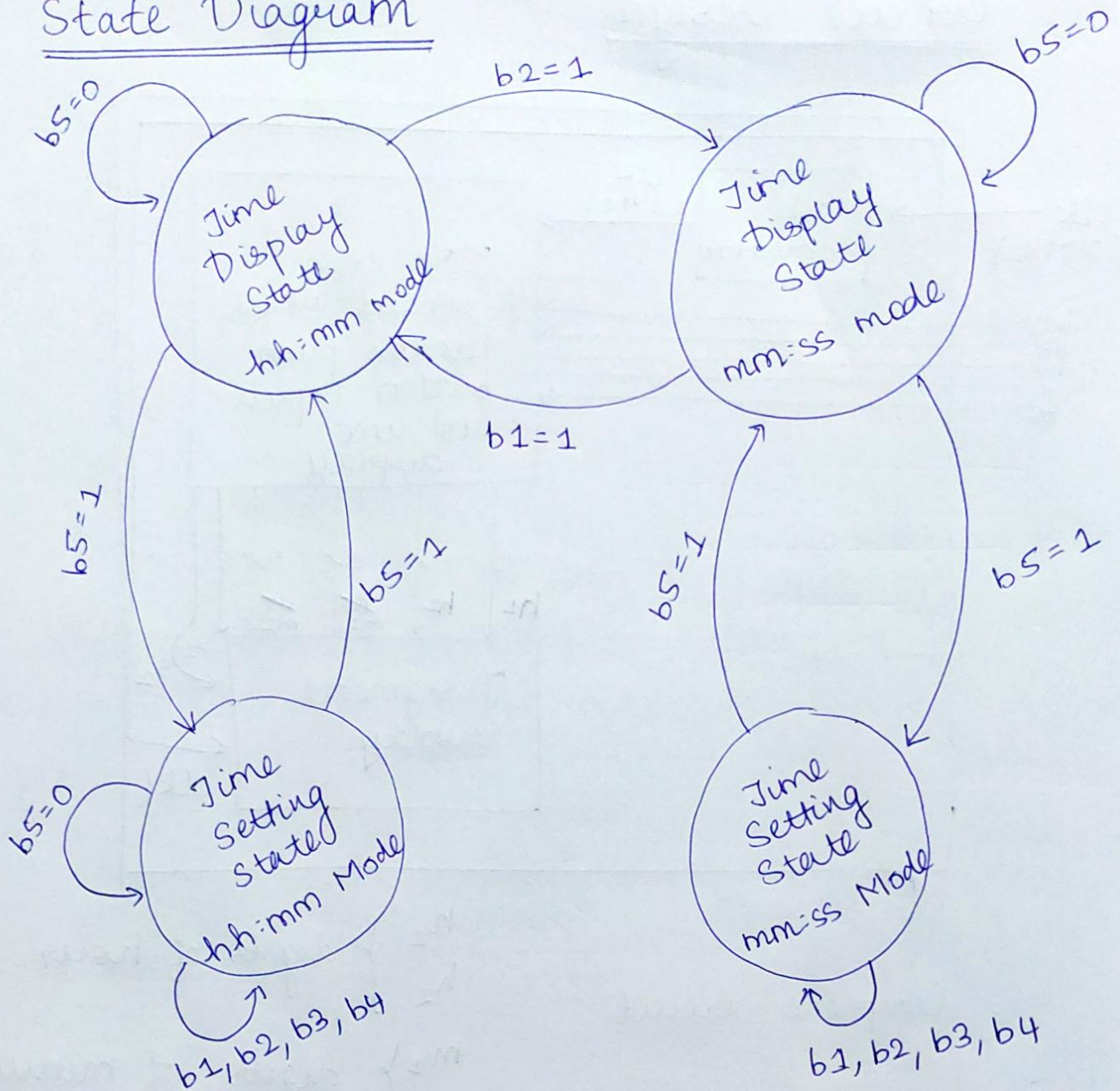

→ Note that b5 is a toggle button


→ Status of all buttons is checked at rising edge of master clock

→ But time is changed at rising edge of converted clock of frequency 1 Hz

→  $b1, b2, b3, b4$  are time setting buttons  
~~for time~~



# Circuit Design

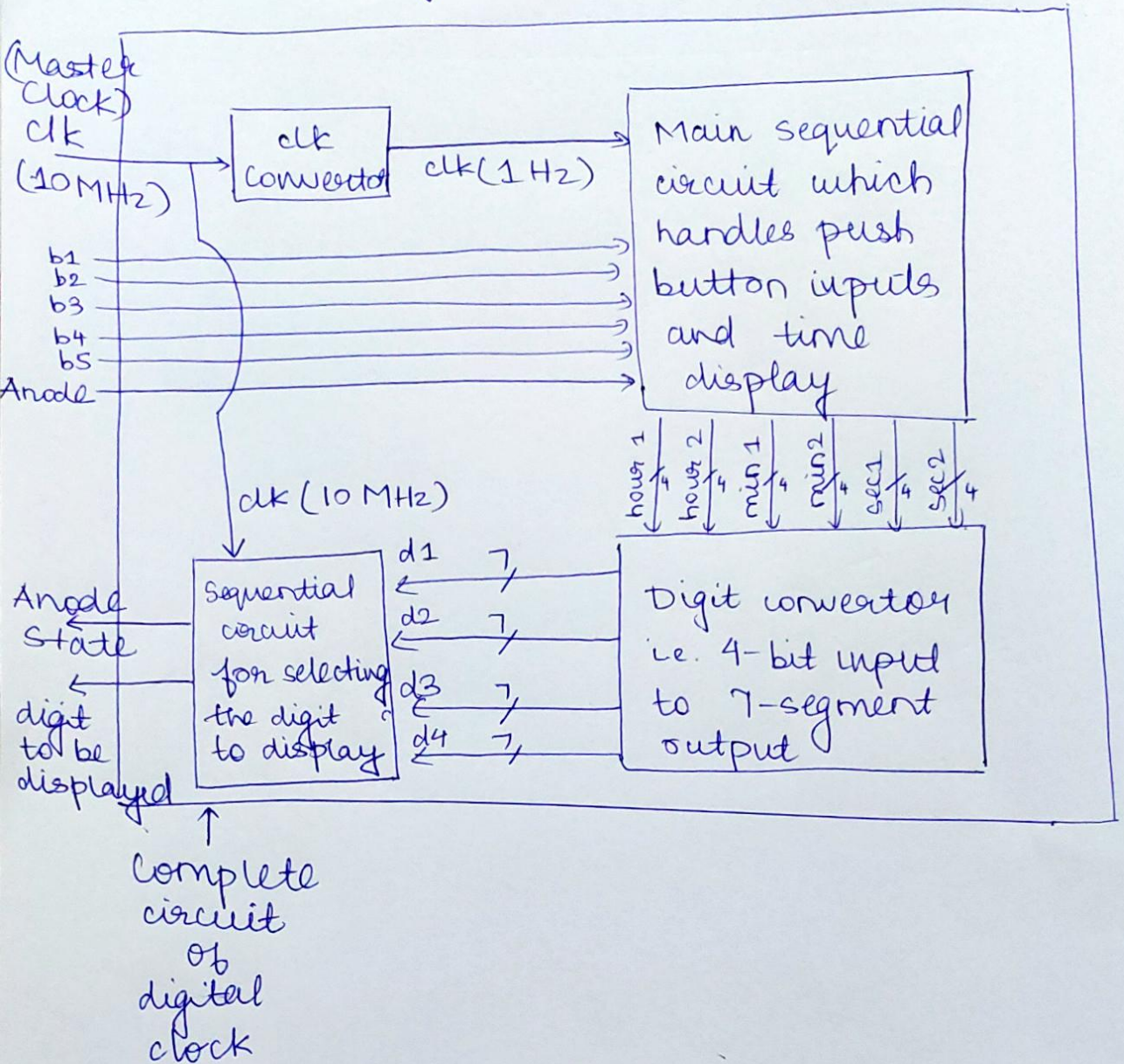

→ Note the final digit displayed as output has a refresh period of